

Name of Student: _____

Scholar No.: _____

INDIAN INSTITUTE OF INFORMATION TECHNOLOGY BHOPAL

Department of Information Technology

Mini Test - 21st August 2025

Subject Name/ Code: COA/IT 3005


MM:10 

Time Allotted: 40 min

NOTE: 1. All questions are compulsory.

2. Answers need to be written in this sheet and submitted. _____

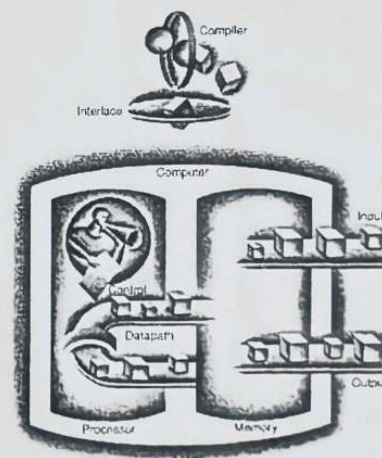1. • Mention 5 **digital logic design** elements used inside the block diagram shown in Fig1.
- Explain each element and its use in one line.
 - Also write which part(s) of the block diagram the element belongs to.



3

Fig1